

Logic Design

A Review



Boolean Algebra

- ❖ Two Values: zero and one
- ❖ Three Basic Functions: And, Or, Not
- ❖ Any Boolean Function Can be Constructed from These Three

And	0	1
0	0	0
1	0	1

Or	0	1
0	0	1
1	1	1

Not	
0	1
1	0



Algebraic Laws

Classification	Law
Identity	$a1=1a=a$ $a+0=0+a=a$
Dominance	$a0=0a=0$ $1+a=a+1=1$
Commutativity	$a+b=b+a$ $ab=ba$
Associativity	$a(bc)=(ab)c$ $a+(b+c)=(a+b)+c$
Distributive	$a(b+c)=ab+ac$ $a+bc=(a+b)(a+c)$
Demorgan's Laws	$(a + b)' = a'b'$ $(ab)' = a' + b'$



Boolean Expressions

- ❖ Addition represents OR
- ❖ Multiplication represents AND
- ❖ Not is represented by a prime a' or an overbar \overline{a}
- ❖ Examples:
 - ❖ $s = a'bc + ab'c + abc' + a'b'c'$
 - ❖ $q = ab + bc + ac + abc$

Superfluous Terms

- ❖ The following Two Equations Represent The Same Function.

$$q = ab + bc + ac + abc$$

$$q = ab + bc + ac$$

a	b	c	q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Prime Implicants

- ❖ A Prime Implicant is a Product of Variables or Their Complements, eg. $ab'cd'$
- ❖ If a Prime Implicant has the Value 1, then the Function has the Value 1
- ❖ A Minimal Equation is a Sum of Prime Implicants



Minimization and Minterms

- ❖ Minimization Reduces the Size and Number of Prime Implicants
- ❖ A MinTerm is a Prime Implicant with the Maximum Number of Variables
- ❖ For a 3-input Function $a'bc$ is a MinTerm, while ab is not.
- ❖ Prime Implicants can be Combined to Eliminate Variables, $abc' + abc = ab$

Minimization with Maps

❖ A Karnaugh Map

		C		B	
		00	01	11	10
A	0	1	0	0	1
	1	1	0	0	0



Procedure

- ❖ Select Regions Containing All 1's
- ❖ Regions should be as Large as Possible
- ❖ Regions must contain 2^k cells
- ❖ Regions should overlap as little as possible
- ❖ The complete set of regions must contain all 1's in the map



Procedure 2

- ❖ Top and Bottom of Map are Contiguous
- ❖ Left and Right of Map are Contiguous
- ❖ Regions represent Prime Implicants
- ❖ Use Variable name guides to construct equation
 - Completely inside the region of a variable means prime implicant contains variable
 - Completely outside the region of a variable means prime implicant contains negation



Applied to Previous Map

		C		B	
		00	01	11	10
A {	0	1	0	0	1
	1	1	0	0	0

$$q=c'b'+c'a'$$



A 4-Variable Karnaugh Map

		D				C	
		00	01	11	10		
B	00	0	0	0	0		
	01	0	1	1	1		
	11	0	1	0	1		
	10	0	1	1	1		



First Minimization

		D		C	
		00	01	11	10
B A	00	0	0	0	0
	01	0	1	1	1
	11	0	1	0	1
	10	0	1	1	1



Second Minimization

		D		C	
		00	01	11	10
B A	00	0	0	0	0
	01	0	1	1	1
	11	0	1	0	1
	10	0	1	1	1



Minimal Forms for Previous Slides:

- ❖ $ab'd + bc'd + a'bc + acd'$

- ❖ $ac'd + a'bd + bcd' + ab'c$

- ❖ Moral: A Boolean Function May Have Several Different Minimal Forms

- ❖ Karnaugh Maps are Ineffective for Functions with More than Six Inputs.



Quine McClusky Minimization

- ❖ Amenable to Machine Implementation
- ❖ Applicable to Circuits with an Arbitrary Number of Inputs
- ❖ Effective Procedure for Finding Prime Implicants, but ...
- ❖ Can Require an Exponential Amount of Time for Some Circuits



Quine-McClusky Procedure

- ❖ Start with The Function Truth Table
- ❖ Extract All Input Combinations that Produce a TRUE Output (MinTerms)
- ❖ Group All MinTerms by The Number of Ones They Contain
- ❖ Combine Minterms from Adjacent Groups



More Quine-McClusky

- ❖ Two Min-Terms Combine If They Differ by Only One Bit
- ❖ The Combined MinTerm has an x in the Differing Position
- ❖ Create New Groups From Combined Min-Terms
- ❖ Each Member of A New Group Must Have the Same Number of 1's and x's



Yet More Quine-McClusky

- ❖ Each Member of A Group Must Have x's in The Same Position.
- ❖ Combine Members of the New Groups To Create More New Groups
- ❖ Combined Terms Must Differ By One Bit, and Have x's in the Same Positions
- ❖ Combine as Much as Possible
- ❖ Select Prime Implicants to “Cover” All Ones in the Function



Quine-McClusky Example 1

Numbers in Parentheses are Truth-Table Positions.

0011(3) 1100(12)
0111(7) 1011(11) 1101(13)
1110(14)
1111(15)

Quine-McClusky Example 2

New Groups After Combining MinTerms

0x11(3,7)	110x(12,13)
1x11(11,15)	111x(14,15)
x011(3,11)	11x0(12,14)
x111(7,15)	11x1(13,15)



Quine-McClusky Example 3

The Final Two Groups

Note That These Two Elements Cover
All Truth-Table Positions

$xx11(3,7,11,15)$


$11xx(12,13,14,15)$

Quine-McClusky Example 4


- ❖ Each Group Element Represents a Prime Implicant
- ❖ It is Necessary to Select Group Elements to Cover All Truth-Table Positions.
- ❖ In This Case, $ab+cd$ is the Minimal Formula.
- ❖ In General, Selecting a Minimal Number of Prime Implicants is NP-Complete




Basic Logic Symbols

 

And

 

Or

 


Not




The Exclusive Or Function

Xor	0	1
0	0	1
1	1	0

 




A Simple Logic Diagram

 





Additional Logic Symbols

 


Nand

 

Nor

 

Buffer

 


Xnor



Sequential Logic

- ❖ Contains Memory Elements
- ❖ Memory is Provided by Feedback
- ❖ Circuit diagrams generally have implicit or explicit cycles
- ❖ Two Styles: Synchronous and Asynchronous

An RS Flip-Flop

 



RS Characteristics


- ❖ If $S=0$ and $R=1$, Q is set to 1, and Q' is reset to 0
- ❖ If $R=0$ and $S=1$, Q is reset to 0, and Q' is set to 1
- ❖ If $S=1$ and $R=1$, Q and Q' maintain their previous state.
- ❖ If $S=0$ and $R=0$, a transition to $S=1$, $R=1$ will cause oscillation.



Instability

- ❖ RS flip-flops can become unstable if both R and S are set to zero.
- ❖ All Sequential elements are fundamentally unstable under certain conditions
 - Invalid Transitions
 - Transitions too close together
 - Transitions at the wrong time

D Flip-Flops

 




D-Flip Flop Characteristics

- ❖ Avoids the instability of the RS flip-flop
- ❖ Retains its last input value
- ❖ Formally known as a “Delay” flip-flop
- ❖ May become unstable if transisions are too close together
- ❖ Is generally implemented as a special circuit, *not* as pictured here.



A Clocked D Flip-Flop

 




Clocked D-Flip Flop Characteristics


- ❖ Synchronizes transisions with a clock
- ❖ Input should remain stable while clock is active
- ❖ Transision at the wrong time can cause instability
 - Changes while clock is active
 - Changes simultaneous with clock

Flip-Flop Symbols

 

Flip-Flop Symbols Contain Implicit Feedback Loops

A CMOS Flip-Flop

 




CMOS Logic Elements

- ❖ CMOS = Complementary MOS
- ❖ CMOS Elements Often Require 2 Clocks or 2 Controls
- ❖ Clocks or Controls must be Complements of One another
- ❖ Clock-Skew (Non-Simultaneous changes in both clocks) can cause problems

An Asynchronous Sequential Circuit

 




Asynchronous Circuits

- ❖ Combinational Logic is used:
 - To Compute New States
 - To Compute Outputs
- ❖ State is maintained in Asynchronous Circuit Elements
- ❖ Care must be used to avoid oscillations

A Synchronous Sequential Circuit

 




Synchronous Circuits

- ❖ Combinational Logic is used to:
 - Compute New States
 - Compute Outputs
- ❖ State is maintained in Synchronous Flip-Flops
- ❖ State Changes can be made only when clock changes
- ❖ Combinational Logic Must be Stable when Clock is Active

Register Symbol

 



Register Issues


- ❖ Generally A Collection of D Flip-Flops
- ❖ Can be Synchronous or Asynchronous
- ❖ Default is Assumption is **Synchronous**
- ❖ May have internal wiring to:
 - Perform Shifts
 - Set/Clear
 - All-Zero Status Flag




Tristate Elements

- ❖ Three States:
 - Zero (Output is grounded)
 - One (Output connected to Power Terminal)
 - High-Impedance (Output Not Connected to Either Power Or Ground)
- ❖ Can be Used to Construct Cheap Multiplexors

CMOS Tri-state Buffers

 


Non-Inverting

 

Inverting


Tri-State Buffer Issues

 - ❖ The Gate Amplifies its Signal
- ❖ May be Inverting or Non-Inverting
- ❖ Often used to Construct Multiplexors Using Wired-Or Connections



More Tri-State Issues

 
- ❖ In a Wired-Or Connection, Only One Buffer can be in Non-Tristate State
- ❖ Violating This Rule Can Destroy The Circuit Due a Power/Ground Short



DANGER!




The CMOS Transmission Gate

 



Transmission Gate Issues

 - ❖ Similar to Tristate Buffer
- ❖ Has No Amplification
- ❖ Number of Consecutive Transmission Gates is Limited
- ❖ Similar Problems With Wired-Or Connections



Logic Design

A Review



Boolean Algebra

- ❖ Two Values: zero and one
- ❖ Three Basic Functions: And, Or, Not
- ❖ Any Boolean Function Can be Constructed from These Three

And	0	1
0	0	0
1	0	1

Or	0	1
0	0	1
1	1	1

Not	
0	1
1	0



Algebraic Laws

Classification	Law
Identity	$a1=1a=a$ $a+0=0+a=a$
Dominance	$a0=0a=0$ $1+a=a+1=1$
Commutativity	$a+b=b+a$ $ab=ba$
Associativity	$a(bc)=(ab)c$ $a+(b+c)=(a+b)+c$
Distributive	$a(b+c)=ab+ac$ $a+bc=(a+b)(a+c)$
Demorgan's Laws	$(a + b)' = a'b'$ $(ab)' = a' + b'$



Boolean Expressions

- ❖ Addition represents OR
- ❖ Multiplication represents AND
- ❖ Not is represented by a prime a' or an overbar \overline{a}
- ❖ Examples:
 - ❖ $s = a'bc + ab'c + abc' + a'b'c'$
 - ❖ $q = ab + bc + ac + abc$

Superfluous Terms

❖ The following Two Equations Represent The Same Function.

$$q = ab + bc + ac + abc$$

$$q = ab + bc + ac$$

a	b	c	q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Prime Implicants

- ❖ A Prime Implicant is a Product of Variables or Their Complements, eg. $ab'cd'$
- ❖ If a Prime Implicant has the Value 1, then the Function has the Value 1
- ❖ A Minimal Equation is a Sum of Prime Implicants



Minimization and Minterms

- ❖ Minimization Reduces the Size and Number of Prime Implicants
- ❖ A MinTerm is a Prime Implicant with the Maximum Number of Variables
- ❖ For a 3-input Function $a'bc$ is a MinTerm, while ab is not.
- ❖ Prime Implicants can be Combined to Eliminate Variables, $abc' + abc = ab$



Minimization with Maps

❖ A Karnaugh Map

		C		B	
		00	01	11	10
A	0	1	0	0	1
	1	1	0	0	0



Procedure

- ❖ Select Regions Containing All 1's
- ❖ Regions should be as Large as Possible
- ❖ Regions must contain 2^k cells
- ❖ Regions should overlap as little as possible
- ❖ The complete set of regions must contain all 1's in the map




Procedure 2

- ❖ Top and Bottom of Map are Contiguous
- ❖ Left and Right of Map are Contiguous
- ❖ Regions represent Prime Implicants
- ❖ Use Variable name guides to construct equation
 - Completely inside the region of a variable means prime implicant contains variable
 - Completely outside the region of a variable means prime implicant contains negation

Applied to Previous Map

		C		B	
		00	01	11	10
A	0	1	0	0	1
	1	1	0	0	0

$$q = c'b' + c'a'$$

 

A 4-Variable Karnaugh Map


		<div>D</div> <div>C</div>			
		00	01	11	10
B	00	0	0	0	0
	01	0	1	1	1
	11	0	1	0	1
	10	0	1	1	1



First Minimization

		D		C	
		00	01	11	10
B A	00	0	0	0	0
	01	0	1	1	1
	11	0	1	0	1
	10	0	1	1	1

Second Minimization

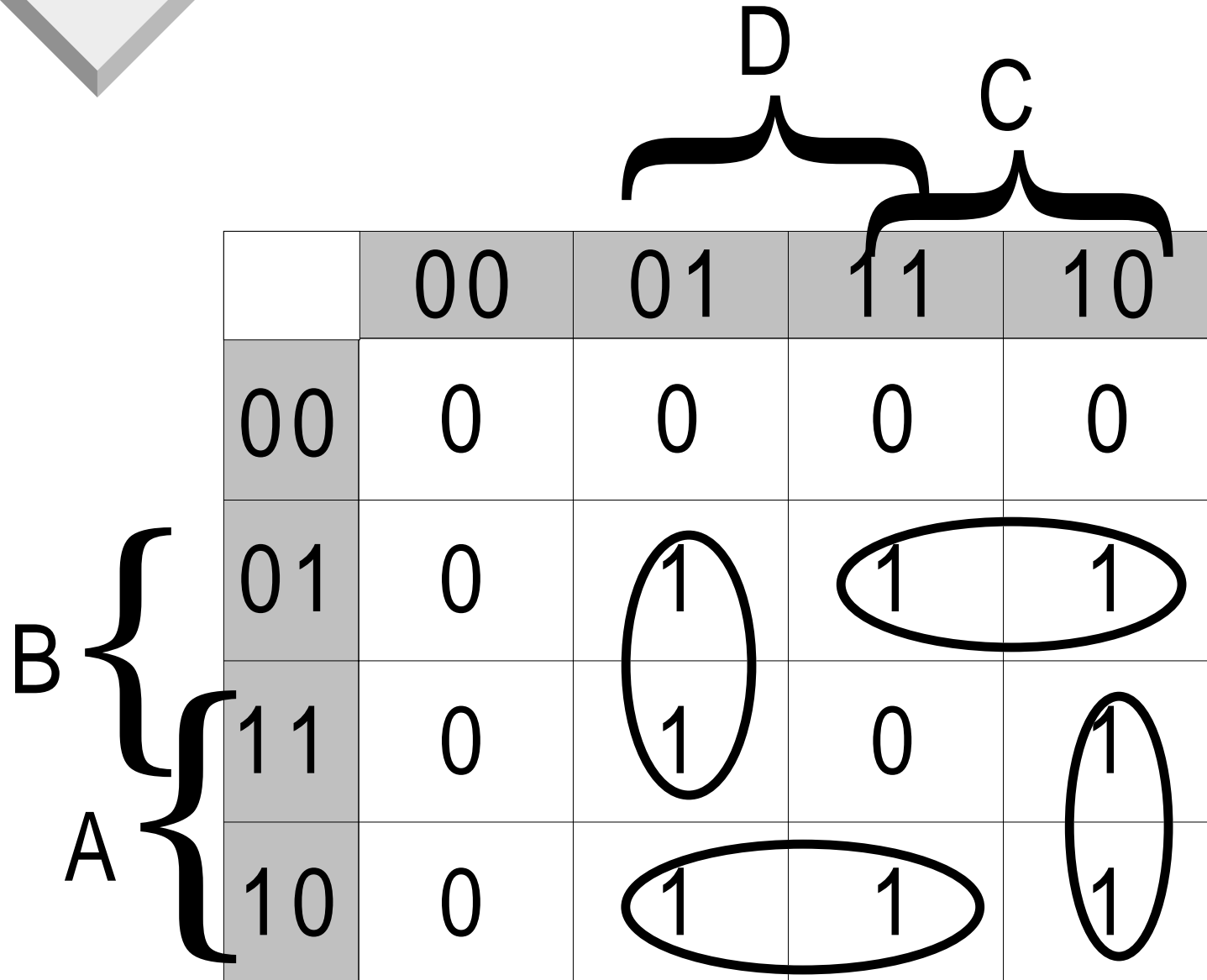

A 4x4 Karnaugh map for a four-variable function. The columns are labeled 00, 01, 11, and 10. The rows are labeled 00, 01, 11, and 10. The map contains 1s in the following cells: (01, 01), (01, 11), (11, 01), (11, 10), (10, 01), and (10, 10). There are three groupings: a horizontal group of four 1s in the middle row (01) labeled 'D' with a brace; a vertical group of two 1s in the second column (01) labeled 'B' with a brace; and a vertical group of two 1s in the fourth column (10) labeled 'A' with a brace. Additionally, there are three pairs of 1s circled: (01, 11) and (11, 01) are circled together; (11, 01) and (11, 10) are circled together; and (10, 01) and (10, 10) are circled together.

	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	0	1	0	1
10	0	1	1	1



Minimal Forms for Previous Slides:

❖ $ab'd + bc'd + a'bc + acd'$

❖ $ac'd + a'bd + bcd' + ab'c$

- ❖ Moral: A Boolean Function May Have Several Different Minimal Forms
- ❖ Karnaugh Maps are Ineffective for Functions with More than Six Inputs.



Quine McClusky Minimization

- ❖ Amenable to Machine Implementation
- ❖ Applicable to Circuits with an Arbitrary Number of Inputs
- ❖ Effective Procedure for Finding Prime Implicants, but ...
- ❖ Can Require an Exponential Amount of Time for Some Circuits



Quine-McClusky Procedure

- ❖ Start with The Function Truth Table
- ❖ Extract All Input Combinations that Produce a TRUE Output (MinTerms)
- ❖ Group All MinTerms by The Number of Ones They Contain
- ❖ Combine Minterms from Adjacent Groups



More Quine-McClusky

- ❖ Two Min-Terms Combine If They Differ by Only One Bit
- ❖ The Combined MinTerm has an x in the Differing Position
- ❖ Create New Groups From Combined Min-Terms
- ❖ Each Member of A New Group Must Have the Same Number of 1's and x's



Yet More Quine-McClusky

- ❖ Each Member of A Group Must Have x's in The Same Position.
- ❖ Combine Members of the New Groups To Create More New Groups
- ❖ Combined Terms Must Differ By One Bit, and Have x's in the Same Positions
- ❖ Combine as Much as Possible
- ❖ Select Prime Implicants to “Cover” All Ones in the Function



Quine-McClusky Example 1

Numbers in Parentheses are Truth-Table Positions.

0011(3) 1100(12)
0111(7) 1011(11) 1101(13)
1110(14)
1111(15)



Quine-McClusky Example 2

New Groups After Combining MinTerms

0x11(3,7)	110x(12,13)
1x11(11,15)	111x(14,15)
x011(3,11)	11x0(12,14)
x111(7,15)	11x1(13,15)



Quine-McClusky Example 3

The Final Two Groups


Note That These Two Elements Cover
All Truth-Table Positions

$xx11(3,7,11,15)$
$11xx(12,13,14,15)$




Quine-McClusky Example 4

 
- ❖ Each Group Element Represents a Prime Implicant
- ❖ It is Necessary to Select Group Elements to Cover All Truth-Table Positions.
- ❖ In This Case, $ab+cd$ is the Minimal Formula.
- ❖ In General, Selecting a Minimal Number of Prime Implicants is NP-Complete




Basic Logic Symbols

 

And

 

Or

 


Not





The Exclusive Or Function

Xor	0	1
0	0	1
1	1	0

 


A Simple Logic Diagram

 


 


Additional Logic Symbols

 


Nand

 

Nor

 

Buffer

 


Xnor




Sequential Logic

- ❖ Contains Memory Elements
- ❖ Memory is Provided by Feedback
- ❖ Circuit diagrams generally have implicit or explicit cycles
- ❖ Two Styles: Synchronous and Asynchronous

An RS Flip-Flop

 

 

RS Characteristics

- ❖ If $S=0$ and $R=1$, Q is set to 1, and Q' is reset to 0
- ❖ If $R=0$ and $S=1$, Q is reset to 0, and Q' is set to 1
- ❖ If $S=1$ and $R=1$, Q and Q' maintain their previous state.
- ❖ If $S=0$ and $R=0$, a transition to $S=1$, $R=1$ will cause oscillation.





Instability

- ❖ RS flip-flops can become unstable if both R and S are set to zero.
- ❖ All Sequential elements are fundamentally unstable under certain conditions
 - Invalid Transitions
 - Transitions too close together
 - Transitions at the wrong time




D Flip-Flops

 

 


D-Flip Flop Characteristics

 - ❖ Avoids the instability of the RS flip-flop
- ❖ Retains its last input value
- ❖ Formally known as a “Delay” flip-flop
- ❖ May become unstable if transisions are too close together
- ❖ Is generally implemented as a special circuit, *not* as pictured here.



A Clocked D Flip-Flop

 





Clocked D-Flip Flop Characteristics

- ❖ Synchronizes transisions with a clock
- ❖ Input should remain stable while clock is active
- ❖ Transision at the wrong time can cause instability
 - Changes while clock is active
 - Changes simultaneous with clock


Flip-Flop Symbols

 

 Flip-Flop Symbols Contain Implicit
Feedback Loops



A CMOS Flip-Flop

 




CMOS Logic Elements

- ❖ CMOS = Complementary MOS
- ❖ CMOS Elements Often Require 2 Clocks or 2 Controls
- ❖ Clocks or Controls must be Complements of One another
- ❖ Clock-Skew (Non-Simultaneous changes in both clocks) can cause problems

An Asynchronous Sequential Circuit

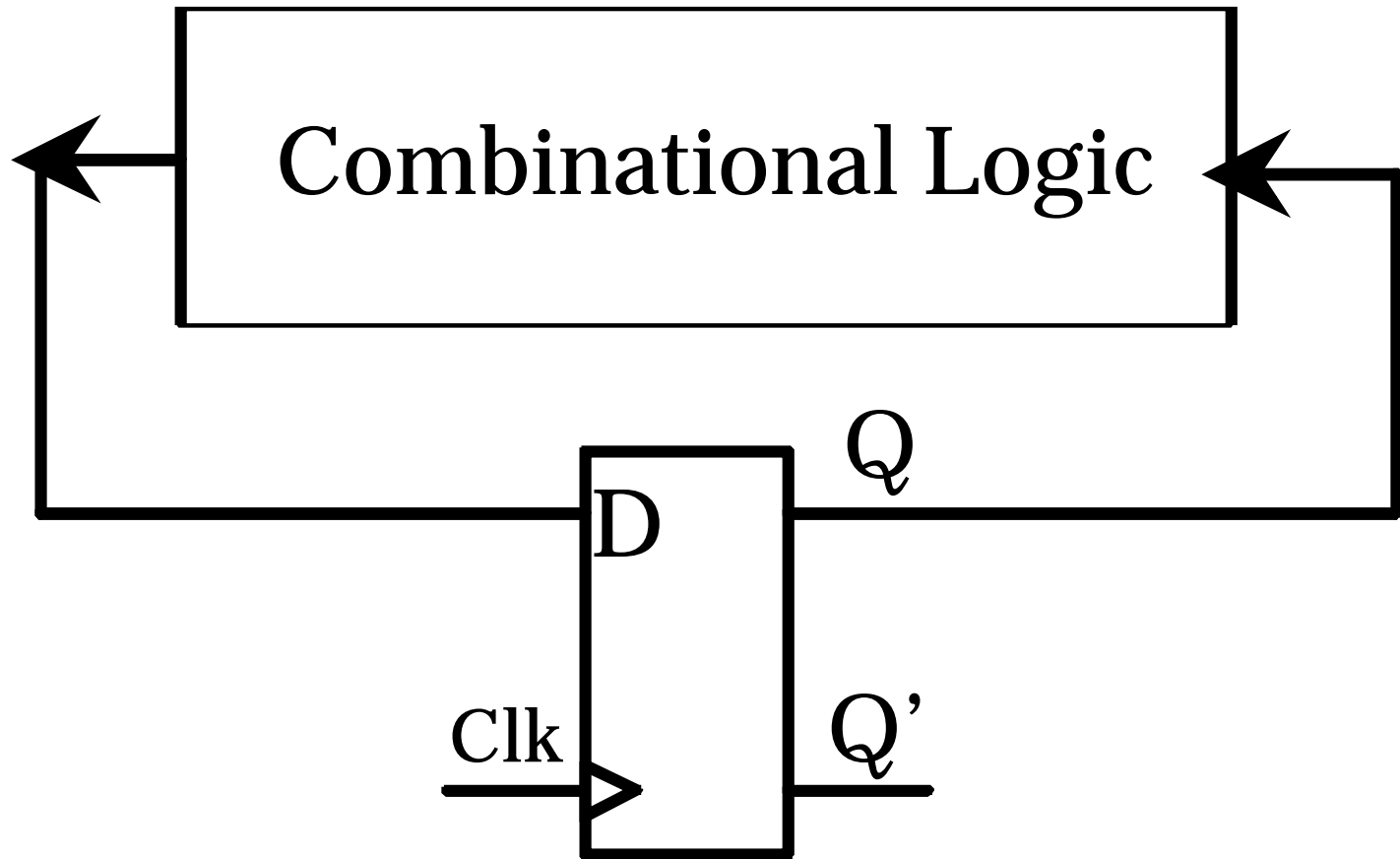





Asynchronous Circuits

- ❖ Combinational Logic is used:
 - To Compute New States
 - To Compute Outputs
- ❖ State is maintained in Asynchronous Circuit Elements
- ❖ Care must be used to avoid oscillations

A Synchronous Sequential Circuit

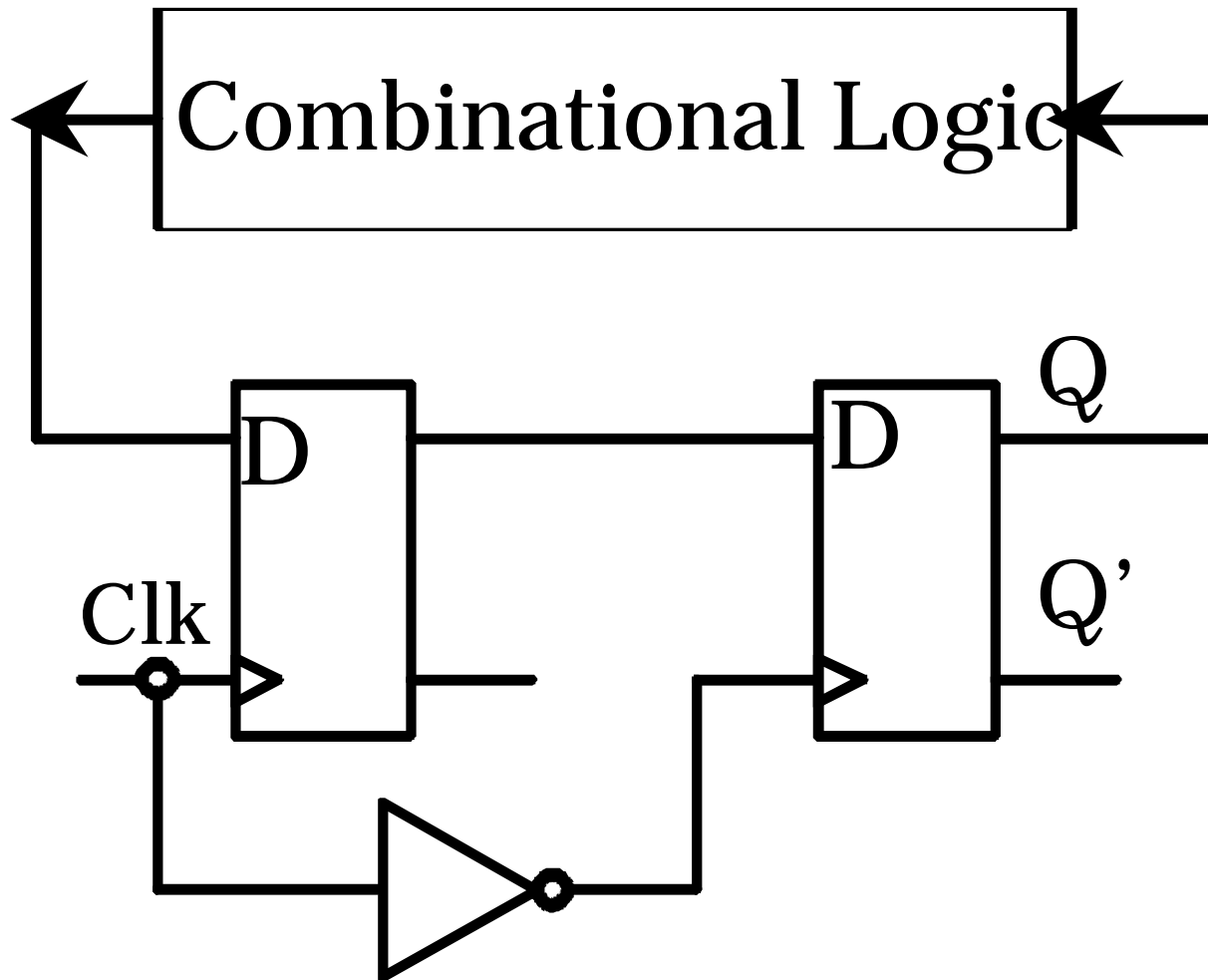

 


Synchronous Circuits

- ❖ Combinational Logic is used to:
 - Compute New States
 - Compute Outputs
- ❖ State is maintained in Synchronous Flip-Flops
- ❖ State Changes can be made only when clock changes
- ❖ Combinational Logic Must be Stable when Clock is Active



Register Symbol

 



Register Issues

- ❖ Generally A Collection of D Flip-Flops
- ❖ Can be Synchronous or Asynchronous
- ❖ Default is Assumption is Synchronous
- ❖ May have internal wiring to:
 - Perform Shifts
 - Set/Clear
 - All-Zero Status Flag




Tristate Elements


- ❖ Three States:
 - Zero (Output is grounded)
 - One (Output connected to Power Terminal)
 - High-Impedance (Output Not Connected to Either Power Or Ground)
- ❖ Can be Used to Construct Cheap Multiplexors



CMOS Tri-state Buffers

 


Non-Inverting

 

Inverting


Tri-State Buffer Issues

 - ❖ The Gate Amplifies its Signal
- ❖ May be Inverting or Non-Inverting
- ❖ Often used to Construct Multiplexors Using Wired-Or Connections



More Tri-State Issues

 
- ❖ In a Wired-Or Connection, Only One Buffer can be in Non-Tristate State
- ❖ Violating This Rule Can Destroy The Circuit Due a Power/Ground Short



DANGER!



The CMOS Transmission Gate

 



Transmission Gate Issues

- ❖ Similar to Tristate Buffer
- ❖ Has No Amplification
- ❖ Number of Consecutive Transmission Gates is Limited
- ❖ Similar Problems With Wired-Or Connections